



MANIPAL UNIVERSITY

DEPARTMENT OF INFORMATION & COMMUNICATION TECHNOLOGY

**MANIPAL INSTITUTE OF TECHNOLOGY
MANIPAL**

Digital Systems Lab [ICT 2163]/ Digital System Design Lab [ICT 2165]

Second Year B. Tech. (IT/CCE) Degree – (2021-22)

INSTRUCTIONS TO THE STUDENTS

- **The students need to report to the labs/departments with clearance card issued by the institute/MAHE. They need to wear mask and gloves in the lab classes.**
- **Students should carry a book for noting observations and required stationeries to every lab session**
- **For every lab, exercise problems have to be solved depicting all design steps in the observation book before coming to the lab.**
- **Be well within the time and must sign in the log register provided**
- **Make sure to occupy the allotted seat and answer the attendance**
- **Show the program/circuit with results to the faculty in charge, on completion of experiments**
- **On receiving approval, copy the program/circuit with obtained results in the lab record**
- **Plagiarism (copying from others) is strictly prohibited and would invite severe penalty in evaluation**
- **Adhere to the rules, follow the institution dress code and maintain the decorum.**

STUDENTS SHOULD NOT

- **Bring mobile phones or any other electronic gadgets to the lab except calculators.**
- **Bring eatables to the lab.**
- **Go out of the lab without permission.**

Lab No	Syllabus covered and list of experiments																																																																																									
Lab 1	Syllabus: K-Map																																																																																									
	<ul style="list-style-type: none">F= XY + Z' (Demonstration)<ol style="list-style-type: none">Simplify the Boolean function 'F' using K maps & implement using NAND gates only F = x'z'+y'z'+yz'+xyz.Design a combinational circuit that accepts a 3 bit number and generates an output binary number equal to the square of the input number. [Hint : Since the maximum 3 bit number is 7, and the square of it is 49, the number of output lines required is 6]. Realize using basic logic gatesTruth Table:<table><tr><th>X</th><th>Y</th><th>Z</th><th>P₅</th><th>P₄</th><th>P₃</th><th>P₂</th><th>P₁</th><th>P₀</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td></td><td></td><td></td><td></td><td></td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td></td><td></td><td></td><td></td><td></td></tr></table>Simplified SOP expressions: Hardware Requirements:	X	Y	Z	P ₅	P ₄	P ₃	P ₂	P ₁	P ₀	0	0	0							0	0	1							0	1	0							0	1	1							1	0	0							1	0	1							1	1	0							1	1	1														
X	Y	Z	P ₅	P ₄	P ₃	P ₂	P ₁	P ₀																																																																																		
0	0	0																																																																																								
0	0	1																																																																																								
0	1	0																																																																																								
0	1	1																																																																																								
1	0	0																																																																																								
1	0	1																																																																																								
1	1	0																																																																																								
1	1	1																																																																																								
Lab 2	Syllabus : Code Converters																																																																																									
	Design following code converters <ol style="list-style-type: none">BCD to excess-3 using NAND gates only Truth Table: <table><tr><th rowspan="2">Decimal</th><th colspan="4">BCD</th><th colspan="4">Excess -3</th></tr><tr><th>A</th><th>B</th><th>C</th><th>D</th><th>W</th><th>X</th><th>Y</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td><td></td><td></td><td></td><td></td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td><td></td><td></td><td></td><td></td></tr><tr><td>2</td><td>0</td><td>0</td><td>1</td><td>0</td><td></td><td></td><td></td><td></td></tr><tr><td>3</td><td>0</td><td>0</td><td>1</td><td>1</td><td></td><td></td><td></td><td></td></tr><tr><td>4</td><td>0</td><td>1</td><td>0</td><td>0</td><td></td><td></td><td></td><td></td></tr><tr><td>5</td><td>0</td><td>1</td><td>0</td><td>1</td><td></td><td></td><td></td><td></td></tr><tr><td>6</td><td>0</td><td>1</td><td>1</td><td>0</td><td></td><td></td><td></td><td></td></tr><tr><td>7</td><td>0</td><td>1</td><td>1</td><td>1</td><td></td><td></td><td></td><td></td></tr></table>	Decimal	BCD				Excess -3				A	B	C	D	W	X	Y	Z	0	0	0	0	0					1	0	0	0	1					2	0	0	1	0					3	0	0	1	1					4	0	1	0	0					5	0	1	0	1					6	0	1	1	0					7	0	1	1	1				
Decimal	BCD				Excess -3																																																																																					
	A	B	C	D	W	X	Y	Z																																																																																		
0	0	0	0	0																																																																																						
1	0	0	0	1																																																																																						
2	0	0	1	0																																																																																						
3	0	0	1	1																																																																																						
4	0	1	0	0																																																																																						
5	0	1	0	1																																																																																						
6	0	1	1	0																																																																																						
7	0	1	1	1																																																																																						

8	1	0	0	0				
9	1	0	0	1				

Hardware Requirements:

2. Self-complementary 8 4 -2 -1 to self-complementary 2 4 2 1 using NOR gates only

Truth Table:

Decimal	8	4	-2	-1	2	4	2	1
	A	B	C	D	W	X	Y	Z
0	0	0	0	0				
1	0	1	1	1				
2	0	1	1	0				
3	0	1	0	1				
4	0	1	0	0				
5	1	0	1	1				
6	1	0	1	0				
7	1	0	0	1				
8	1	0	0	0				
9	1	1	1	1				

Hardware Requirements:

**Lab
3**

Syllabus :Adders , Multipliers

1. Design a full subtractor .
2. Design a 4-bit binary adder/subtractor using 7483 IC and external gates.
3. Design 2 bit X 3 bit binary multiplier using 7483 ICs and external gates.

**Lab
4**

Syllabus Magnitude Comparators and Decoder


1. Design a 1 bit magnitude comparator with cascading inputs using basic gates.

2. Design 5-bit magnitude comparator using 7485 ICs

3. Implement one-bit full adder using 74138 IC and external NAND gates only.


The truth table of 1-bit full adder is given below. The circuit diagram using the 74138 and NAND gates is shown below.

Input bit for number A	Input bit for number B	Carry bit input C _{IN}	Sum bit output S	Carry bit output C _{OUT}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Lab 5 Syllabus MUX, Flip Flops

 1. Design a 4:1 MUX using basic logic gates.



Select Lines		Output (Y)
S ₁	S ₀	
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

2. Design a combinational circuit using 74151 IC and external gates to implement the following functions.

$$F_1(w,x,y,z) = wx'y'z + w'xy'z \quad F_2(w,x,y,z) = xz' + wx'y$$

3. Convert a given D flip flop to work as a JK flip flop.

Lab 6 Syllabus : Asynchronous and Synchronous counters

1. Design a counter that performs UP count from 00 to 81 using 7490 IC and external gates.

2. Design an asynchronous counter that counts from 00h to 24H using 7493 IC and external gates.

- | | |
|--|--|
| | <p>3. Design a 2-bit binary UP/DOWN counter such that when control input $Y=0$, it performs BINARY UP count and when $Y=1$,</p> |
|--|--|

Lab 7	Syllabus : Sequence Generators and Shift Registers

- 2. Design a 4 - bit universal shift register using D flip flops and 74153 ICs**

Select Lines	Function performed
--------------	--------------------

Select Lines		Function performed
S₁	S₀	F
0	0	No change
0	1	Left Shift
1	0	Right Shift
1	1	Parallel Load

Hardware Requirements:

- ### Hardware Requirements:

Hardware Requirements:

Q_D	Q_C	Q_B	Q_A

Lab	Syllabus : Sequence Detectors
8	

1. Design a sequential model that detects the sequence 1011 using T flip flops and external gates. Assume that overlapping sequence is to be detected.

State Table with T flip flop excitation

Present State			Input	Next State			D flip flop input			Output
				X = 0			X = 0			
Q _C	Q _B	Q _A	X	Q _C ⁺	Q _B ⁺	Q _A ⁺	T _C	T _B	T _A	Y
0	0	0	0							
0	0	0	1							
0	0	1	0							
0	0	1	1							
0	1	0	0							
0	1	0	1							

0	1	1	0								
0	1	1	1								
1	0	0	0								
1	0	0	1								
1	0	1	0								
1	0	1	1								
1	1	0	0								
1	1	0	1								
1	1	1	0								
1	1	1	1								

- 2. Design a sequential model that detects the sequence 101 using JK Flip Flop. Assume non overlapping sequence is to be detected.**